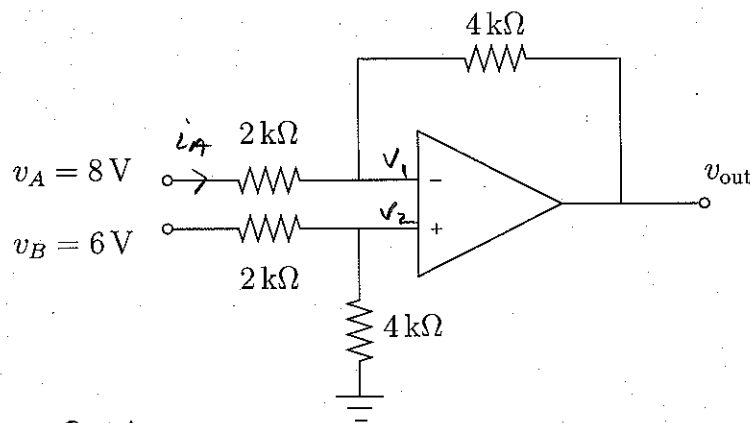


PHYS 235 — Exam #2
Thursday, March 5, 2009

Name: KEY

1. (18 pts) Consider the illustrated circuit containing an ideal op-amp (powered from $\pm 15\text{V}$ supplies) and resistors. Determine the numerical value of output voltage v_{out} . Be sure to include all reasoning and/or derivations.



Negative feedback $\Rightarrow v_2 = v_1$

$$v_2 = \frac{4}{2+4} \cdot v_B = \frac{4}{6} \times 6 = 4\text{V}$$



$$\Rightarrow v_1 = 4\text{V}$$

$$i_A = \frac{\Delta V}{2\text{k}\Omega} = \frac{8-4}{2\text{k}\Omega} = 2\text{mA}$$

$$v_{\text{out}} = v_1 - i_A \times 2 = 4 - 2 \times 4 = -4\text{V}$$

2. (18 pts)

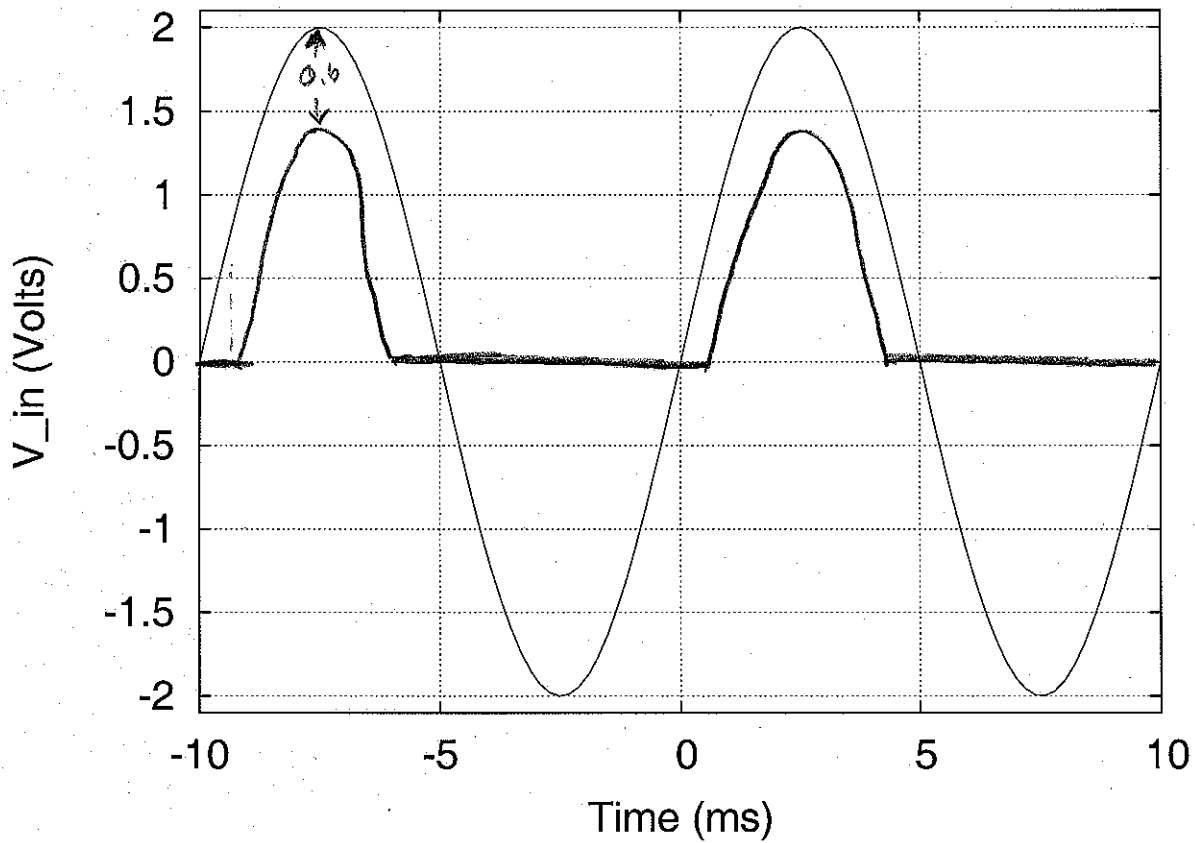
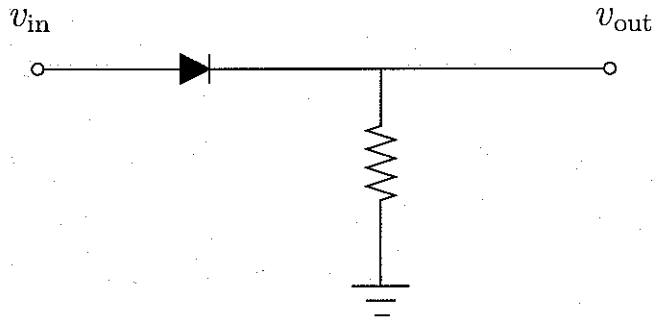
- (a) Consider the illustrated circuit with an ideal silicon diode and a resistor, and the illustrated input signal v_{in} . Sketch the output signal you would observe on an oscilloscope. (Draw your sketch on the same set of axes as the input.)



When forward biased $V_{out} = V_{in} - 0.6V$

When reversed biased $i_R = 0 \Rightarrow V_{out} = 0$

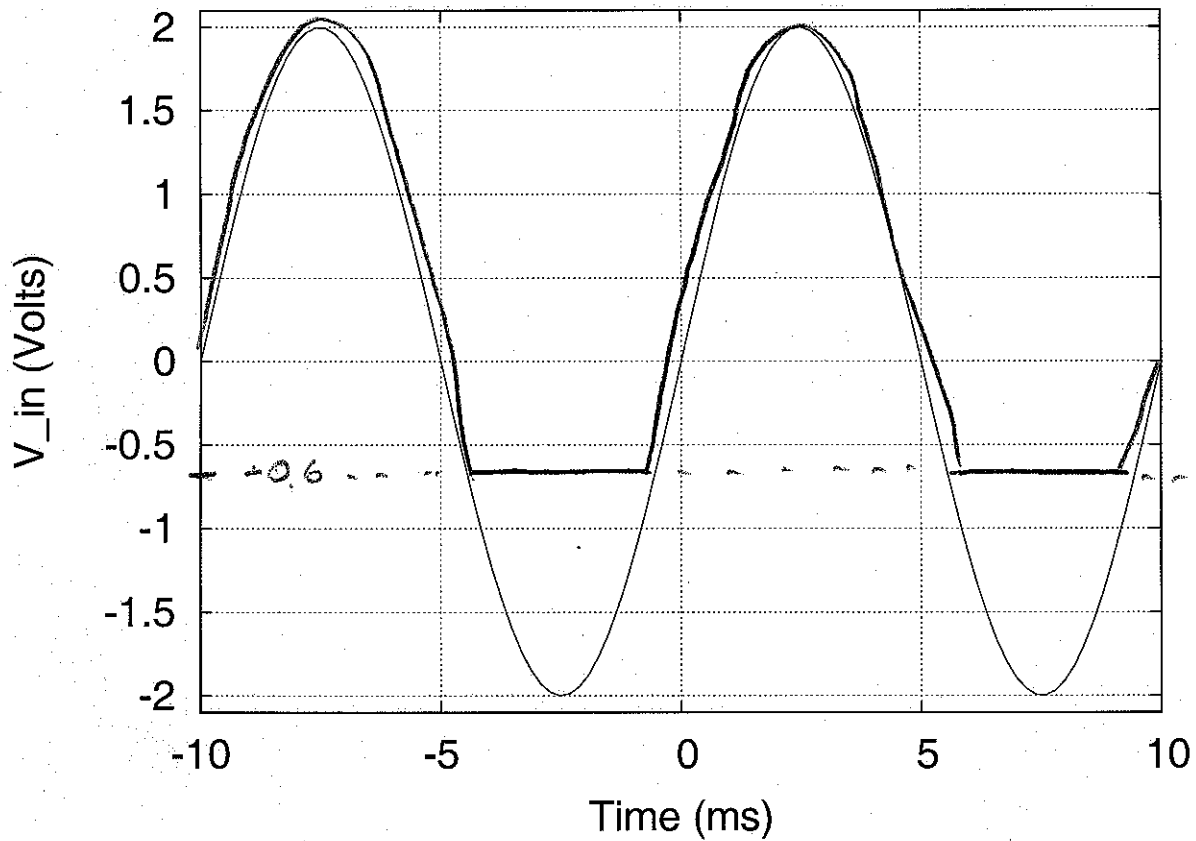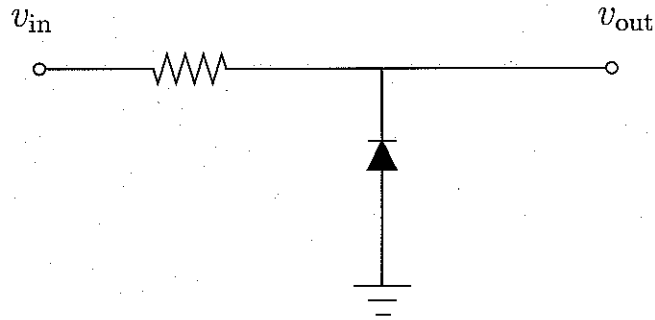- (b) Consider the illustrated circuit with an ideal silicon diode and a resistor, and the illustrated input signal v_{in} . Sketch the output signal you would observe on an oscilloscope. (Draw your sketch on the same set of axes as the input.)




When forward biased $V_{out} = 0 - 0.6 = -0.6V$

When reverse biased $i_R = 0 \Rightarrow V_{out} = V_{in}$

3. (10 pts) Why is an amplifier with a voltage gain of 1, i.e., with $v_{out} = v_{in}$, of any use to anyone? (Specific examples may help your explanation.)


An amplifier with a gain of 1 can be very useful if it has a high input impedance and a low output impedance. This can turn a poor voltage source into a much better approximation of an ideal voltage source, where the output voltage is (approximately) independent of the current drawn from the source.

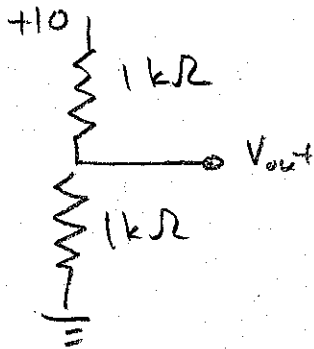Example: Consider the following voltage divider.



For $R_{load} \gg 1k\Omega$ $V_{out} \approx 5V$
 but for $R_{load} \approx 500\Omega$ $V_{out} \approx 2.5V$
 Not a great voltage source!


Fix:

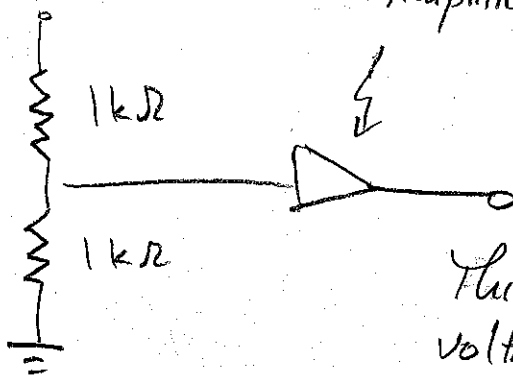

Amplifier with $R_{input} \gg 1k\Omega$, say $1M\Omega$
 $R_{output} \sim 10\Omega$
 Gain = 1

This will give a constant voltage output of 5V down to load resistances near 10Ω .

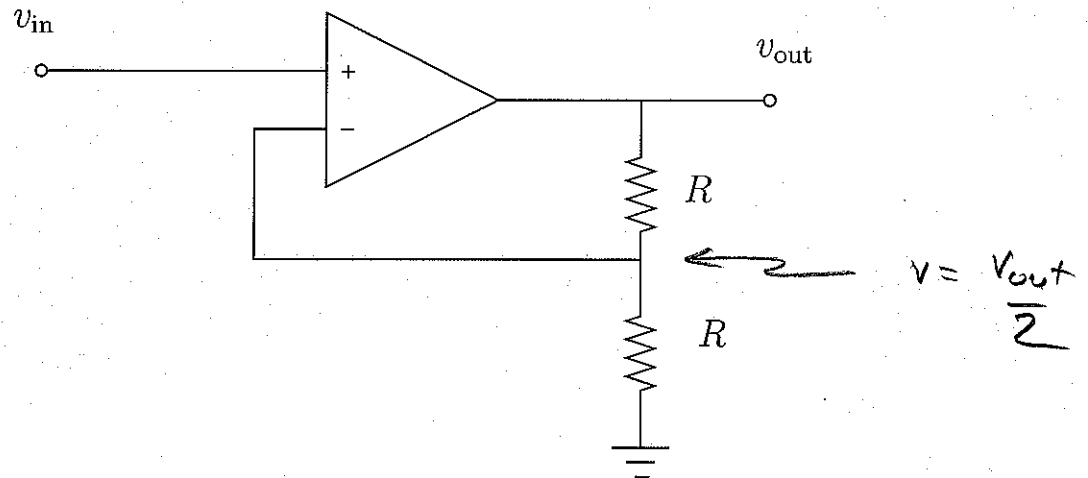4. (a) Assume that the op-amp is ideal and determine an expression for the gain of the illustrated circuit.
- (b) Assume the that illustrated op-amp is **not** ideal in one respect: the open-loop gain A_0 is **not** infinite. Determine an expression for the gain of the circuit. (This result should reduce to your previous result in the limit $A_0 \rightarrow \infty$.)



a) Negative feedback $\Rightarrow v_2 = v_1$

or $v_{in} = \frac{v_{out}}{2}$

$\Rightarrow v_{out} = 2v_{in}$

b)

$$v_{out} = A_0(v_2 - v_1)$$

$$= A_0(v_{in} - \frac{1}{2}v_{out})$$


$$= A_0 v_{in} - \frac{1}{2}A_0 v_{out}$$

$\Rightarrow v_{out}(1 + \frac{1}{2}A_0) = A_0 v_{in}$

$$v_{out} = \frac{A_0}{1 + \frac{1}{2}A_0} v_{in} = \frac{2A_0}{2 + A_0} v_{in}$$

$\xrightarrow{A_0 \rightarrow \infty} 2v_{in}$ ✓

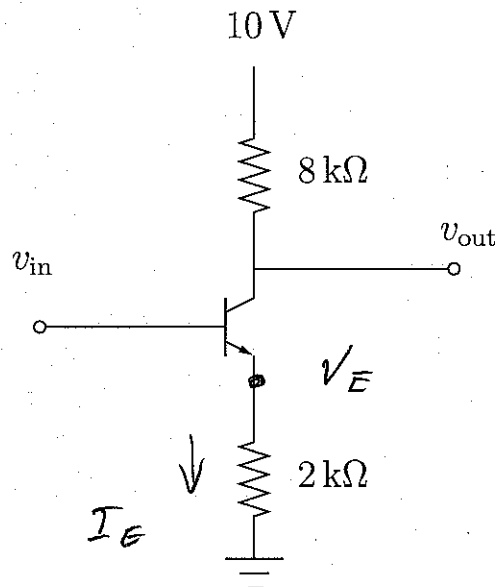5. (18 pts) Consider the illustrated circuit with a transistor and two resistors. You may use the "simplest" model of transistor behavior in this problem, i.e., $I_B \simeq 0$.



- (a) Determine the output when $v_{in} = 2\text{ V}$.
 (b) Determine the output when $v_{in} = 4\text{ V}$.

$$a) \quad V_E = v_{in} - 0.6 = 1.4$$

$$I_E = \frac{V_E}{2\text{ k}\Omega} = 0.7\text{ mA}$$

$$\begin{aligned} V_{out} &= 10 - I_C \times 8\text{ k}\Omega \\ &= 10 - I_E \times 8\text{ k}\Omega \\ &= 10 - 0.7\text{ mA} \times 8\text{ k}\Omega \\ &= 10 - 5.6\text{ V} \\ &= 4.4\text{ V} \end{aligned}$$


$$b) \quad \text{Rules would give } I_E = \frac{3.4\text{ V}}{2\text{ k}\Omega} = 1.7\text{ mA}$$

$$\begin{aligned}V_{out} &= 10 - I_E \times 8 \text{ k}\Omega \\ &= 10 - 1.7 \text{ mA} \times 8 \text{ k}\Omega \\ &= 10 - 13.6 \\ &= -3.6 \text{ V}\end{aligned}$$



But this is impossible. The low potential end of the emitter resistor can't go below 0, nor can anything else in the collector-emitter chain, so

$$(V_{out})_{min} \approx 0$$

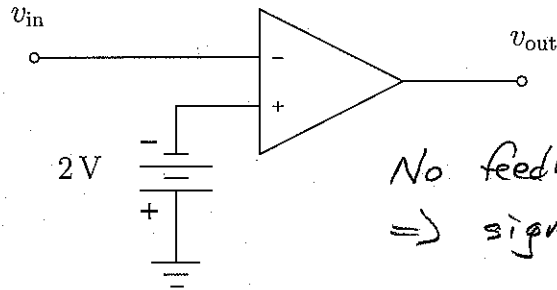6. (18 pts) Sketch the output of the illustrated circuit for the given input.



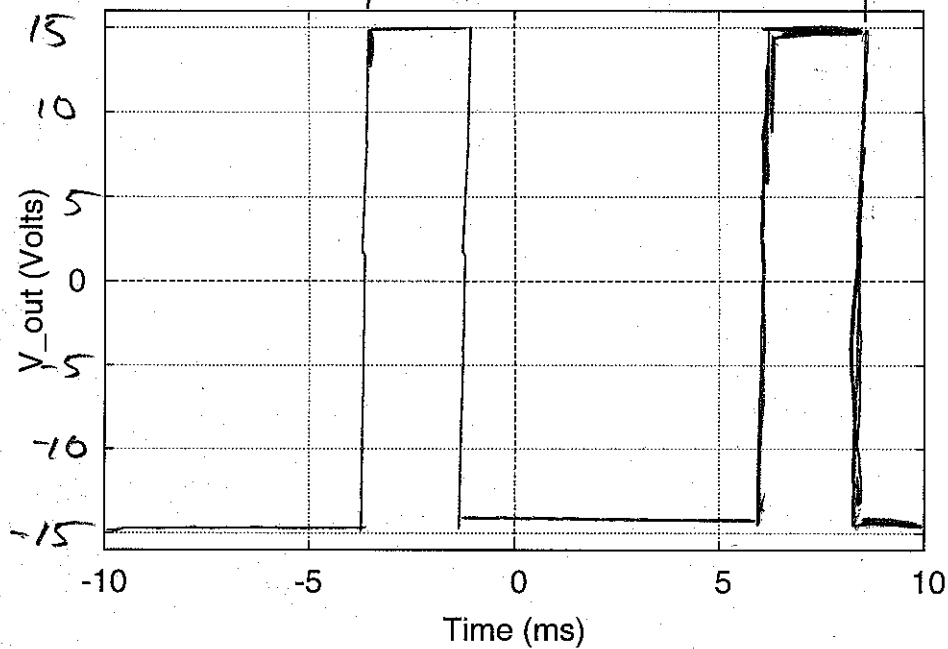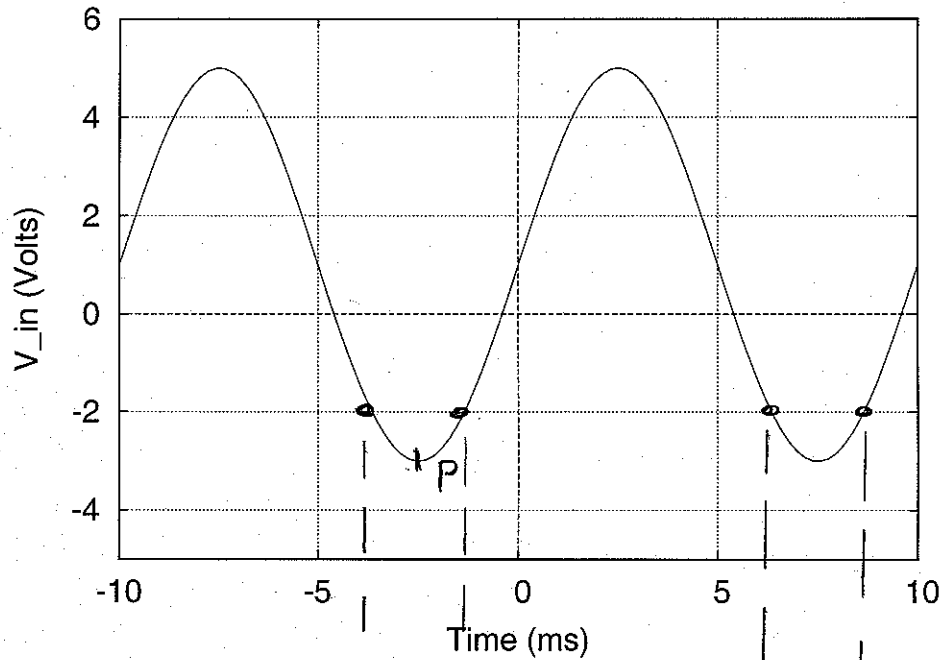No feedback
 \Rightarrow signal w/ clipping



At P $V_{out} = A_o [-2 - (-3)] = +A_o \rightarrow$ Positive saturation