

Logic operations

- We have already seen keywords `or`, `and`, `not` used in Python
 - Had a specific purpose – Boolean expressions. For example:

```
if x >= 0 and x < 10:
    print("x is a single digit")
```

- Python has a set of operators for bitwise computations:
 - `&`: bitwise AND
 - `|`: bitwise OR
 - `~`: bitwise NOT
 - `>>`: shift to the right
 - `<<`: shift to the left

LOGIC OPERATIONS

A *bit* of intuition...

```
21 << 1      5 & 6      5 | 6
 42          ?          ?
```

```
21 >> 1
10
```

A *bit* of intuition...

Sometimes the bits are *almost* visible:

```
10101      101 110      101 110
21 << 1    5 & 6      5 | 6
```

```
10101      000
21 >> 1    ~0
```

A *bit* of intuition...

Sometimes the bits are *almost* visible:

```
10101      101 110      101 110
21 << 1    5 & 6      5 | 6
101010    100
```

```
10101      000
21 >> 1    ~0
1010      111
```

However `~0` gives -1 ???

```
>>> x = 0
>>> ~x
-1
```

We will see a thorough discussion on this later. Here is a quick illustration of the idea.

Binary	Decimal
000	0
001	1
010	2
011	3
100	-4
101	-3
110	-2
111	-1

Take an example of 3-bit binary number. We can represent 8 different values.

If we want to represent negative numbers, we would typically (for good reasons!) to have $-(n+1)$ to n . In this case, -4 to 3. In this system, the binary pattern of -1 is 111, which is `~0`.

Truth tables

input		output	input		output	input		output
x	y	AND (x,y)	x	y	OR (x,y)	x	NOT (x)	
0	0	0	0	0	0	0	1	
0	1	0	0	1	1	1	0	
1	0	0	1	0	1			
1	1	1	1	1	1			

AND outputs 1 only if **ALL** inputs are 1

OR outputs 1 if **ANY** input is 1

NOT reverses its input

All computation

... consists of functions of bits, or *boolean values*

Boolean inputs x, y, \dots can *only* be 0 or 1 (False or True).

Boolean functions can output *only* 0 or 1 (False, True).

inputs		output
x	y	fn (x, y)
0	0	0
0	1	1
1	0	1
1	1	0

Truth table

Lots of bits!

inputs			output
x	y	z	fn (x, y, z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Truth table

LOGIC GATES AND CIRCUITS

Reviewing...

- We have:
 - explored a wide range of data types
 - learned how different encodings are used for different types
 - learned that, at the core of all data stored in the computer are bits
 - observed different operations that can be performed on these bits (AND, OR, NOT)


We have one **BIG QUESTION** remaining...

HOW IS COMPUTATION ACTUALLY CARRIED OUT?

In a computer, each bit is represented as a **voltage** (1 is +5v and 0 is 0v)

Computation is simply the deliberate combination of those voltages!

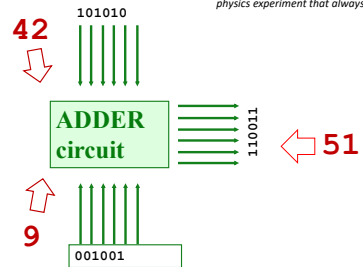
Feynman: Computation is just a physics experiment that always works!



In a computer, each bit is represented as a voltage (1 is +5v and 0 is 0v)


Computation is simply the deliberate combination of those voltages!

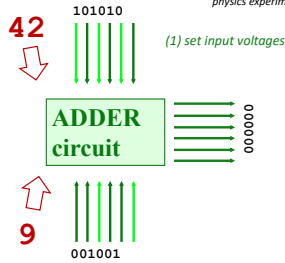Feynman: Computation is just a physics experiment that always works!



In a computer, each bit is represented as a voltage (1 is +5v and 0 is 0v)

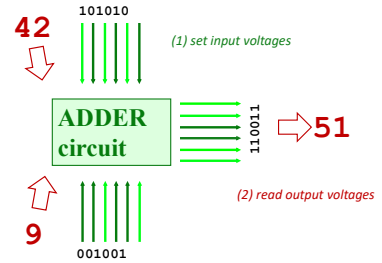
Computation is simply the deliberate combination of those voltages!



In a computer, each bit is represented as a voltage (1 is +5v and 0 is 0v)


Computation is simply the deliberate combination of those voltages!

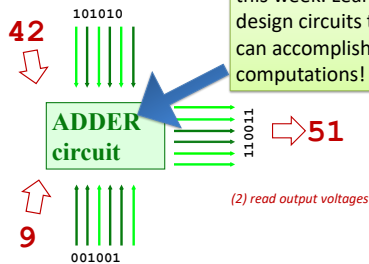HOW? The focus for this week: Learn to design circuits that can accomplish simple computations!




We need only three building circuits to compute anything at all

input		output	input		output	input		output
x	y	AND (x, y)	x	y	OR (x, y)	x	NOT (x)	
0	0	0	0	0	0	1	0	
0	1	0	0	1	1	0	1	
1	0	0	1	0	1	1	0	
1	1	1	1	1	1	1	0	

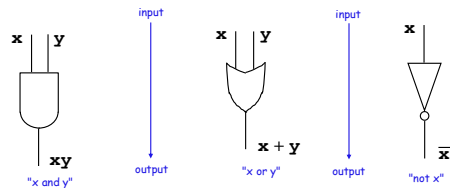

Circuits from logic gates... ?

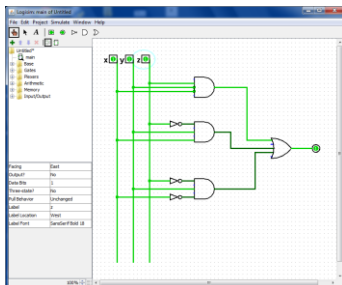

What are all of the inputs that make this circuit output 1? Note the three input gates, both OR and AND gates.

Logisim

- HW 5 – Use **Logisim** (a free circuit simulation package) to design circuits to perform simple computations
- Hard? Well, let's recall our claim – we only need AND, OR and NOT to compute anything at all...

Constructive Proof !

i Specify a **truth table** defining **any** function you want

input		output
x	y	fn(x, y)
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *only for that specific input!*

iii **OR** them all together



Minterm Expansion Principle – algorithm for building expressions from truth tables

Minterm expansion readily converts into logic gates...

Constructive Proof !


i Specify a **truth table** defining **any** function you want

input		output
x	y	fn(x, y)
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *only for that specific input!*

iii **OR** them all together

$$\overline{x}y + x\overline{y}$$

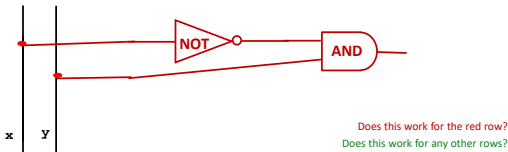

Constructive Proof !


i Specify a **truth table** defining **any** function you want

input		output
x	y	fn(x, y)
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *only for that specific input!*

iii **OR** them all together

$$\overline{x}y + x\overline{y}$$

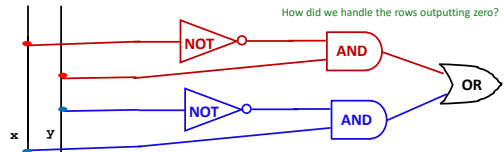


Constructive Proof !

i Specify a **truth table** defining **any** function you want

input		output
x	y	fn(x, y)
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *only for that specific input!*

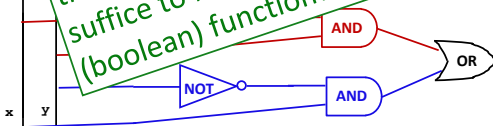This is a constructive proof that AND, OR, and NOT suffice to build any (boolean) function!



Constructive Proof !


i Specify a **truth table** defining **any** function you want

input		output
x	y	fn(x, y)
0	0	0
0	1	1
1	0	1
1	1	0

ii For each input row whose output needs to be 1, build an **AND** circuit that outputs 1 *only for that specific input!*

But... **ALL** functions are just boolean functions: binary!

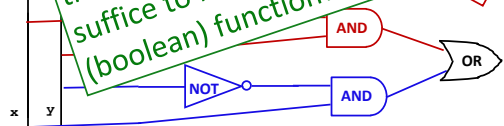This is a constructive proof that AND, OR, and NOT suffice to build any (boolean) function!



EXAMPLE

