

Remember the steps ...

- Build the truth table
- Construct the minterm expression
- Convert the minterm expression into circuits

MORE EXAMPLE

"English"

$f(x, y)$ should output 1 when either x or y is 1, but not both, otherwise, output 0

XOR

1

input		output
x	y	XOR (x, y)
0	0	0
0	1	1
1	0	1
1	1	0


2

Formula

$$\bar{x}y + x\bar{y}$$

Minterm Expansion Principle – algorithm for building expressions from truth tables

3

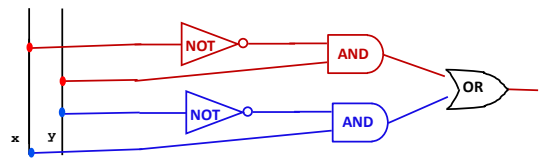

Addition as a circuit

- You (hopefully!) will build a simple adder circuit in lab...

input Output:

Addition as a circuit

- You (hopefully!) will build a simple adder circuit in lab...

input			output: SUM	
x	y	c _{in}	c _{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

A full adder sums three bits. (A 2-bit adder is a half adder)


Share the inputs, but design separate circuits for each output bit...

Building a Full Adder

Implementing addition in silicon...?

Create a circuit for each output bit!

input			output: SUM	
x	y	c _{in}	c _{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

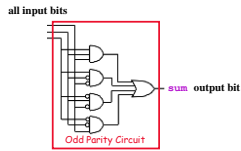


Building a Full Adder

Implementing addition in silicon...?

Create a circuit for each output bit!

input			output: SUM	
x	y	c _{in}	c _{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

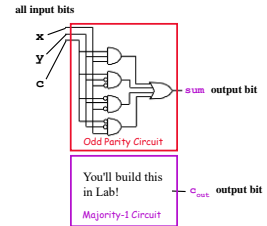


Building a Full Adder

Implementing addition in silicon...?

Create a circuit for each output bit!

input			output: SUM	
x	y	c _{in}	c _{out}	sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

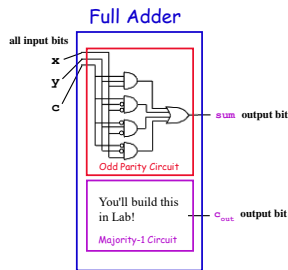


Composing circuits

4-bit Ripple-carry Adder

two 4-bit inputs

	0	1	1	1
+	1	1	0	1
<hr/>				

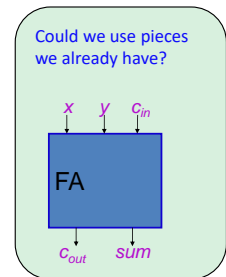

How many output bits?


Getting rid of ANDs ?

Can you get rid of the ANDs by using only NOTs and ORs?

input		output
x	y	AND(x, y)
0	0	0
0	1	0
1	0	0
1	1	1


input		output	output	output
x	y	OR(x, y)	NOT(OR(x, y))	NOT(OR(NOT(x), NOT(y)))
0	0	0	1	0
0	1	1	0	0
1	0	1	0	0
1	1	1	0	1

AND... without ANDs

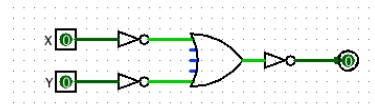

NOR

input		output
x	y	NOR (x, y)
0	0	1
0	1	0
1	0	0
1	1	0

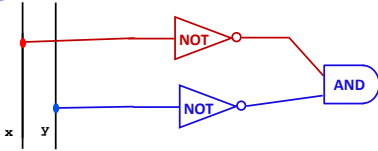

NOR gates

- NOR gates

input		output
x	y	NOR (x, y)
0	0	1
0	1	0
1	0	0
1	1	0


no AND, OR, NOT!



- FACT: ALL gates can be built out of NOR gates...

15

NOR equivalencies

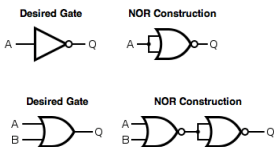


NOT

OR

What about AND?

16

AND... with NORs

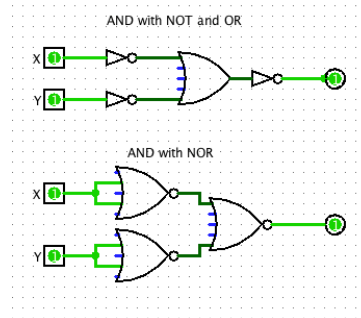


17

Odd parity circuit

- Here's the truth table defining a function

input			output
x	y	z	odd(x, y, z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

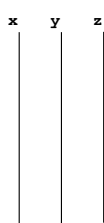

Create NOT "trails" ... if you want to...

Let's build an odd parity circuit


- Build separate circuits for each output-1 row using ANDs and NOTs. Combine them with an OR.

- Write down minterm expansion formula that represents this circuit?

Odd parity circuit

- Here's the truth table defining a function

input			output
x	y	z	odd(x, y, z)
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

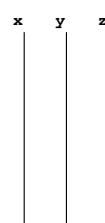


Create NOT "trails" ... if you want to...

Let's build an odd parity circuit

- Build separate circuits for each output-1 row using ANDs and NOTs. Combine them with an OR.

- Write down minterm expansion formula that represents this circuit?

Odd parity circuit

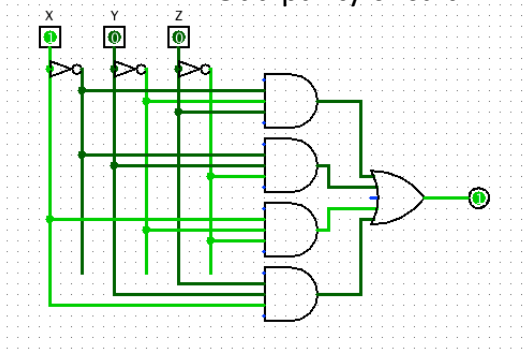

20