

## Policies and Review Topics for Exam #2

The following policies will be in effect for the exam. They will be included in a list of instructions and policies on the first page of the exam:

1. You will be allowed to use a non-wireless enabled calculator, such as a TI-89.
2. You will be allowed to use two 8.5 × 11-inch two-sided handwritten help sheets. No photocopied material or copied and pasted text or images are allowed. If there is a table or image from the textbook or some other source that you feel would be helpful during the exam and that is not included on the table and formula sheet that I will provide, please notify me.
3. All help sheets will be collected at the end of the exam but will be returned to you later.
4. If you begin the exam after the start time, you must complete it in the remaining allotted time. However, you may not take the exam if you arrive after the first student has completed it and left the room. The latter case is equivalent to missing the exam.
5. **You may not leave the exam room without prior permission except in an emergency or for an urgent medical condition. Please use the restroom before the exam.**

The following is a list of topics that could appear in one form or another on the exam. Not all of these topics will be covered, and it is possible that an exam problem could cover a detail not specifically listed here. However, this list has been made as comprehensive as possible. **You should be familiar with the topics on the review sheet for the previous exam as well.**

Although significant effort has been made to ensure that there are no errors in this review sheet, some might nevertheless appear. The textbook is the final authority in all factual matters, unless errors have been specifically identified there. You are ultimately responsible for obtaining accurate information when preparing for the exam.

Voltage/current maxima/minima on loaded transmission lines

- expressions for  $|\tilde{V}(z)|$  and  $|\tilde{I}(z)|$  and their derivations

$$|\tilde{V}(z)| = |V_0^+| \left[ 1 + |\Gamma|^2 + 2|\Gamma| \cos(\theta_r + 2\beta z) \right]^{1/2}$$

$$|\tilde{I}(z)| = \frac{|V_0^+|}{Z_0} \left[ 1 + |\Gamma|^2 - 2|\Gamma| \cos(\theta_r + 2\beta z) \right]^{1/2}$$

- voltage maxima (current minima) occur where  $\cos(\theta_r + 2\beta z) = +1$
- voltage minima (current maxima) occur where  $\cos(\theta_r + 2\beta z) = -1$
- voltage maxima and minima separated by  $\lambda/4$
- current maxima and minima separated by  $\lambda/4$
- voltage and current maxima and minima repeat every  $\lambda/2$
- voltage maxima and current maxima separated by  $\lambda/4$
- For the coordinate system we are using, physically meaningful values of  $z$  are negative, and physically meaningful values of  $d$  (or  $l$ ) are positive.
- VSWR,  $d_{\max}$ , and/or  $d_{\min}$  on a mismatched line ( $Z_L \neq Z_0$ ) can be used to find  $Z_L$  (basis of operation of slotted line)

Transmission line impedance calculations

- electrical length (in degrees, radians, or wavelengths) vs. physical length (in cm, m, etc.)
- input impedance of lossless line with load:

$$Z_{in}(-l) = Z_0 \frac{Z_L + jZ_0 \tan(\beta l)}{Z_0 + jZ_L \tan(\beta l)}$$

- sometimes useful alternate form:  $Z_{in}(-l) = \frac{\tilde{V}(-l)}{\tilde{I}(-l)} = Z_0 \frac{1 + \Gamma e^{-j2\beta l}}{1 - \Gamma e^{-j2\beta l}}$

- open-circuit load ( $Z_L = \pm\infty$ ):  $Z_{in}(-l) = -jZ_0 \cot(\beta l)$

if  $l \ll \lambda$ , then  $Z_{in}(-l) = \frac{-jZ_0}{\tan(\beta l)} \approx \frac{-jZ_0}{\beta l} = -j\sqrt{\frac{L'}{C'}} \frac{1}{(\omega\sqrt{L'C'})l} = \frac{1}{j\omega C'l}$

- short-circuit load ( $Z_L = 0$ ):  $Z_{in}(-l) = jZ_0 \tan(\beta l)$

if  $l \ll \lambda$ , then  $Z_{in}(-l) \approx jZ_0\beta l = j\sqrt{\frac{L'}{C'}}(\omega\sqrt{L'C'})l = j\omega L'l$

- matched line ( $Z_L = Z_0$ ):  $Z_{in}(-l) = Z_0$

- quarter-wave matching section ( $l = \lambda/4$ ):  $Z_{in}(-l) = \frac{Z_0^2}{Z_L}$

- half-wave section ( $l = n\lambda/2$ ): impedances repeat every  $\lambda/2$  along line

- purely reactive loads ( $Z_L = jX$ ):  $|\Gamma| = 1$ ;  $Z_{in}$  is purely imaginary

- “electrically short” lines (i.e.,  $l \ll \lambda$ ):  $Z_{in} \approx Z_L$ ; this is the “circuit theory” limit; valid only if  $Z_0 \gg |Z_L \tan(\beta l)|$  and  $|Z_L| \gg |Z_0 \tan(\beta l)|$  (i.e., denominator of formula for  $Z_{in}$  above is dominated by  $Z_0$  and numerator is dominated by  $Z_L$ )

- differences between  $Z_0$  and  $Z_{in}$  and  $Z_L$

- VSWR along line (especially along matching sections) changes at transitions, such as changes in  $Z_0$  or locations where a device or component (such as an  $R$ ,  $L$ ,  $C$ , or antenna) is connected in parallel or in series with the line

- lossy lines:  $Z_{in}(-l) = Z_0 \frac{Z_L + Z_0 \tanh(\gamma l)}{Z_0 + Z_L \tanh(\gamma l)}$ , where  $\gamma = \alpha + j\beta$  and  $Z_0$  is complex

- calculation of  $V_0^+$  and/or  $\tilde{V}_{in}$ , and the meanings of the two quantities

textbook formula:  $V_0^+ = \tilde{V}_g \left( \frac{Z_{in}}{Z_g + Z_{in}} \right) \left( \frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right)$  and  $\tilde{V}_{in} = \tilde{V}_g \left( \frac{Z_{in}}{Z_g + Z_{in}} \right)$

alternate formula:  $V_0^+ = \tilde{V}_g \frac{Z_0}{(Z_0 + Z_g)e^{j\beta l} + (Z_0 - Z_g)\Gamma e^{-j\beta l}}$  (useful when  $Z_{in} = 0$ )

Note: if  $Z_g = Z_0$ , then  $V_0^+ = \frac{1}{2} \tilde{V}_g e^{-j\beta l}$

- determination of total phasor or time-domain voltage or current at specific locations along line or their components [i.e.,  $\tilde{V}_{fwd}(z)$  and  $\tilde{V}_{ref}(z)$  or  $\tilde{I}_{fwd}(z)$  and  $\tilde{I}_{ref}(z)$ ]

- cascaded line sections (one follows another) of different characteristic impedances

- equivalent impedance at junction of two or more line sections (i.e., “shunt” connections)

- input impedance when loads/devices are placed at different locations along line (not just at the end)

### Impedance matching

- typical goals of impedance matching:
  - o maximum power transfer
  - o specific load impedance required for proper operation of signal source
  - o to prevent reflections
  - o combination of two or more of the above
- quarter-wave matching sections (characteristic impedance =  $Z_{0Q}$ )
  - o if  $Z_L$  is purely real and target matching impedance  $Z_{in}$  is purely real (latter is usually the case), use a quarter-wave section with  $Z_{0Q} = \sqrt{Z_{in}Z_L}$
  - o for complex loads:
    - can connect stub at load to cancel any load reactance (susceptance)
    - alternatively, can find location of voltage max (at  $z = -d_{max}$ ) or min (at  $z = -d_{min}$ ), where  $Z_{in}$  is purely real ( $n = \text{integer}$ ):

$$\text{voltage max: } \theta_r - 2\beta d_{max} = 2\pi n \text{ and } Z(-d_{max}) = Z_0 \frac{1+|\Gamma|}{1-|\Gamma|}$$

$$\text{voltage min: } \theta_r - 2\beta d_{min} = (2n+1)\pi \text{ and } Z(-d_{min}) = Z_0 \frac{1-|\Gamma|}{1+|\Gamma|}$$

if matching to main line of characteristic impedance  $Z_0$ , use

$$Z_{0Q} = \sqrt{Z(-d_{max})Z_0} \text{ or } Z_{0Q} = \sqrt{Z(-d_{min})Z_0}$$

- definitions of admittance, conductance, and susceptance:  $Y = G + jB$ , where  $Y = 1/Z$
- $B = -1/X$  for a pure reactance or susceptance
- $G = 1/R$  for a pure resistance or conductance
- wave admittance:  $Y_{in}(-l) = Y_0 \frac{Y_L + jY_0 \tan(\beta l)}{Y_0 + jY_L \tan(\beta l)}$  and  $Y_{in}(-l) = Y_0 \frac{1 - \Gamma e^{-j2\beta l}}{1 + \Gamma e^{-j2\beta l}}$
- shunt-element matching **[not covered on exam]**

- o an “element” is typically a capacitor, inductor, or stub (usually a stub)
- o place element at a location where  $\text{Re}\{Y_{in}\} = Y_0 = 1/Z_0$
- o two possible locations every  $\lambda/2$ :  $l_{main}^{shunt} = \frac{\lambda}{4\pi} [\theta_r \pm \cos^{-1}(-|\Gamma|)]$ , where  $\Gamma = |\Gamma|e^{j\theta_r}$
- o can also use any location  $n\lambda/2$  away from those given by formula ( $n = \text{integer}$ )
- o input susceptances at those points are given by

$$B_{in}^{shunt} = \text{Im}\{Y_{in}(-l_{main}^{shunt})\} = \pm \frac{2|\Gamma|}{\sqrt{1-|\Gamma|^2}} Y_0$$

“+” solution to  $l_{main}$  formula corresponds to “+” solution to  $B_{in}$  formula

- o set  $B_{stub} = -B_{in}$

- series-element matching (usually L or C)
  - o place element at a location where  $\text{Re}\{Z_{in}\} = Z_0$
  - o two possible locations every  $\lambda/2$ :  $l_{main}^{series} = \frac{\lambda}{4\pi} [\theta_r \pm \cos^{-1}(|\Gamma|)]$
  - o can also use any location  $n\lambda/2$  away from those given by formula ( $n = \text{integer}$ )
  - o input reactances at those points are given by
 
$$X_{in}^{series} = \text{Im}\{Z_{in}(-l_{main}^{series})\} = \mp \frac{2|\Gamma|}{\sqrt{1-|\Gamma|^2}} Z_0$$
 “+” solution to  $l_{main}$  formula corresponds to “-” solution to  $X_{in}$  formula
  - o set  $X_{element} = -X_{in}$
- short- or open-circuited stubs cancel input susceptance  $B_{in}$  or input reactance  $X_{in}$ 
  - o goal is to make  $B_{stub} = -B_{in}$  or  $X_{stub} = -X_{in}$
  - o short-circuited stub:  $l_{stub,sc} = \frac{\lambda}{2\pi} \tan^{-1}\left(\frac{X_{stub,sc}}{Z_0}\right) = \frac{\lambda}{2\pi} \tan^{-1}\left(\frac{-Y_0}{B_{stub,sc}}\right)$
  - o open-circuited stub:  $l_{stub,oc} = \frac{\lambda}{2\pi} \tan^{-1}\left(\frac{B_{stub,oc}}{Y_0}\right) = \frac{\lambda}{2\pi} \tan^{-1}\left(\frac{-Z_0}{X_{stub,oc}}\right)$
- add  $\lambda/2$  if formula for  $l_{main}$  or  $l_{stub}$  gives a negative length (arises from the  $360^\circ$  ambiguity with the  $\tan^{-1}$  and  $\cos^{-1}$  functions)
- use care when evaluating  $\tan^{-1}$ ; check quadrant!
- can use lumped-element ( $C$  and/or  $L$  only) matching networks instead of stubs in many cases (usually at low microwave frequencies and below)
- $Z_0$  of stub does not have to equal  $Z_0$  of main line, but it usually does
- be able to find VSWR along stub, along line between matching element and load, and along line between signal source and matching element (requires the calculation of  $\Gamma$  at various points)

Relevant course material:

HW: #3 and #4

Reading: Assignments from Jan. 29 through Feb. 19, including the supplemental reading: “Impedance Matching Using Single Transmission Line Stubs”

This exam will focus primarily on the course outcomes listed below and related topics:

1. Predict voltages, currents, and/or power flow along a transmission line given the line parameters and the signal source and load connected to the line.
2. Design a transmission line-based impedance matching system.

The course outcomes are listed on the Course Policies and Information sheet, which was distributed at the beginning of the semester and is available on the Syllabus and Policies page at the course web site. The outcomes are also listed on the Course Description page. Note, however, that some topics not directly related to the course outcomes could be covered on the exam as well.