

LABORATORY 12


Multiplexers and Flip-Flops

In the first part of this lab, we will learn how to use the 74153 4-line to 1-line multiplexer chip. Besides serving as a data selector, we will see how to use the 74153 to implement the 3-input majority function and a serial-to-parallel converter. In the second part of the lab, we will investigate a simple and widely-used device that acts as a 1-bit memory, the S-R flip-flop. (The S-R flip-flop is the foundation of the D flip-flop.) You can read about both topics in Chapter 12 of Bobrow.

You can use switches and LEDs for your inputs and outputs, respectively.

Multiplexer

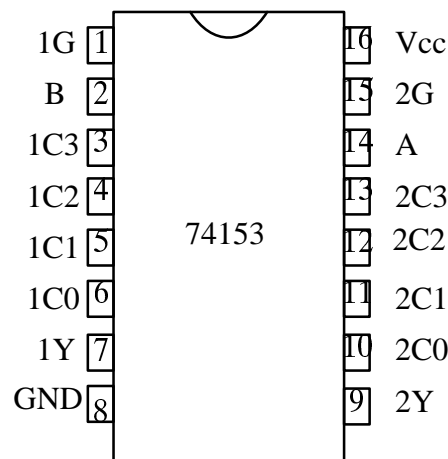The 74153 contains two 4-line to 1-line multiplexers. A multiplexer is a device that connects one of four input lines (C0, C1, C2, C3) to a single output line (Y) as specified by two selector bits (B and A). There is also a “strobe” input (G) that must be set to “0” in order for the multiplexer to function properly. A pin diagram for the 74153 is shown below.



In your lab notebook, record the output Y that you measure for each input in the following truth table. The X means that the input is irrelevant to the output. Verify by inputting both “0” and “1” for some of the X’s. Do you see how this chip functions as a multiplexer/data selector?

| <u>Select</u> | | <u>Data Inputs</u> | | | | <u>Strobe</u> | <u>Output</u> |
|---------------|---|--------------------|----|----|----|---------------|---------------|
| B | A | C0 | C1 | C2 | C3 | G | Y |
| X | X | X | X | X | X | 1 | |
| 0 | 0 | 0 | X | X | X | 0 | |
| 0 | 0 | 1 | X | X | X | 0 | |
| 0 | 1 | X | 0 | X | X | 0 | |
| 0 | 1 | X | 1 | X | X | 0 | |
| 1 | 0 | X | X | 0 | X | 0 | |
| 1 | 0 | X | X | 1 | X | 0 | |
| 1 | 1 | X | X | X | 0 | 0 | |
| 1 | 1 | X | X | X | 1 | 0 | |