

## Step and Natural Responses for RC and RL Circuits

For RC and RL circuits, the step and natural responses are obtained by solving a first-order, linear differential equation with constant coefficients and constant “input” (or forcing function),

$$\frac{dx}{dt} + ax(t) = b,$$

where  $a$  and  $b$  are constants, and the initial value  $x(t_0)$  is known. The solution is

$$x(t) = \left[ x(t_0) - \frac{b}{a} \right] e^{-a(t-t_0)} + \frac{b}{a}, \quad \text{for } t > t_0.$$

The function  $x(t)$  may be either a voltage or a current in the circuit. Note that the time constant is

$$\tau = \frac{1}{a}.$$

It is useful to write the equation in words:

$$x(t) = [\text{initial value} - \text{final value}] \cdot \exp\left(-\frac{t - \text{starting time}}{\text{time constant}}\right) + \text{final value},$$

for  $t >$  the starting time. We can often obtain the “initial value,” “final value,” and “time constant” using circuit analysis, and then we can immediately write the solution from the previous equation.

**Important note:** The “initial value” refers to time  $t = t_0^+$ , i.e., the instant *after* a change occurs in the circuit (such as switches opening or closing).