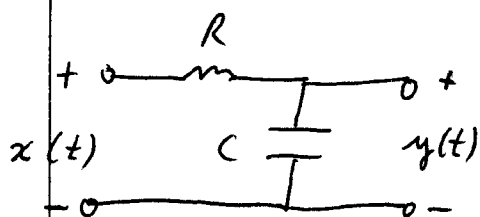


Laplace Transform Applied to Linear Systems



$$x(t) = 0 \text{ for } t < 0$$

$y(0^-)$ = Initial capacitor voltage

Recall that
$$\frac{dy}{dt} + \frac{1}{RC} y(t) = \frac{1}{RC} x(t)$$

Laplace transform of differential equation:

Exercise:


Find $y(t)$ if $RC = 10^{-3}$, $y(0) = -1V$, $x(t) = 2u(t)$.

Let us focus on the "zero state response" (ZSR) = output due to input signal with zero "initial conditions".

Circuits can be drawn in the s -domain:

$$R \rightarrow R, \quad C \rightarrow \frac{1}{sC}, \quad L \rightarrow sL$$

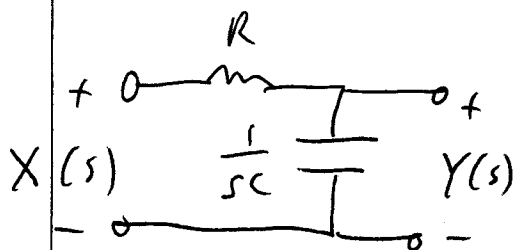[See pages 400-406 of the Lathi text for derivation and how non-zero initial conditions can be included]



$$\begin{aligned} Y(s) &= \frac{\frac{1}{sC}}{R + \frac{1}{sC}} X(s) \\ &= \frac{X(s)}{1 + (RC)s} = \frac{\frac{1}{RC}}{s + \frac{1}{RC}} X(s) \end{aligned}$$

(Can also see this from differential eq.)

Important Definition: "Transfer function"

$$H(s) = \frac{Y(s)}{X(s)} = \frac{\text{Laplace transform of output}}{\text{Laplace transform of input}}$$

$$= \frac{\frac{1}{RC}}{s + \frac{1}{RC}} \text{ for RC circuit.}$$

∴ $Y(s) = H(s) \cdot X(s)$ [for ZSR]

Laplace transform property }

Multiplication in s-domain



Convolution in time-domain.

$$y(t) = \boxed{h(t)} * x(t)$$

↑ What must $h(t)$ be? _____


∴ Transfer function $H(s) = \mathcal{L}\{ \quad \}$

What is the impulse response of RC circuit?

** NOTE: Impulse response $h(t) \neq \frac{y(t)}{x(t)}$.




But in s-domain: $H(s) = \frac{Y(s)}{X(s)}$

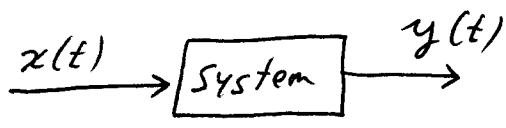Exercises: Find the transfer function $H(s)$ of the following linear, time-invariant systems.



① Ideal integrator
 $y(t) = \int_0^t x(\lambda) d\lambda$

② Differentiator
 $y(t) = \frac{dx}{dt}$

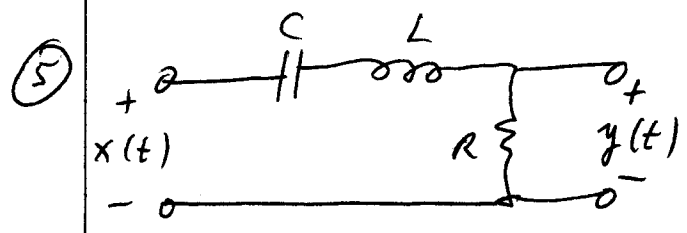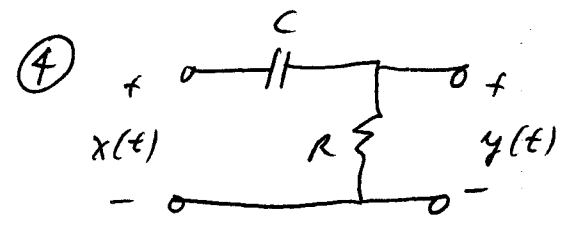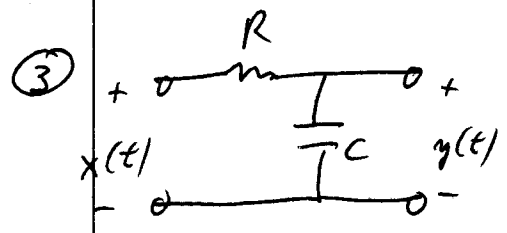




Usually transfer function $H(s) = \frac{\text{Numerator polynomial}}{\text{Denom. polynomial}}$

"ZEROS" of system = roots of numerator of $H(s)$

"POLES" of system = roots of denominator of $H(s)$

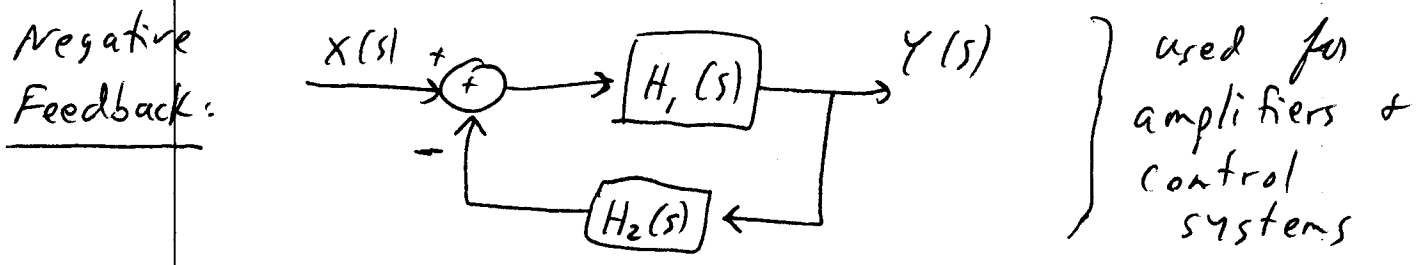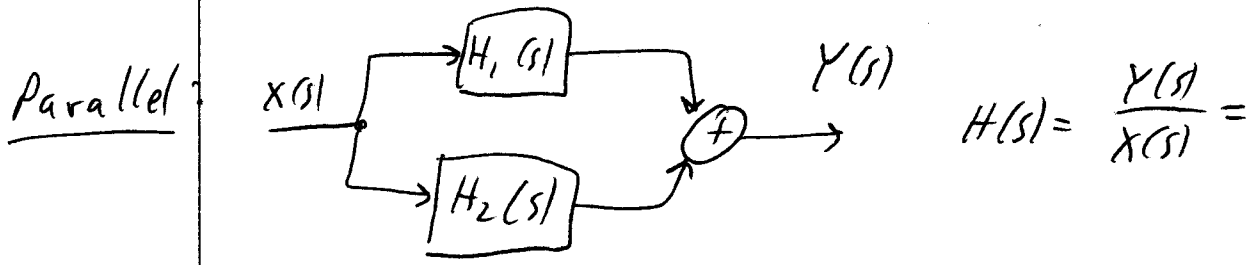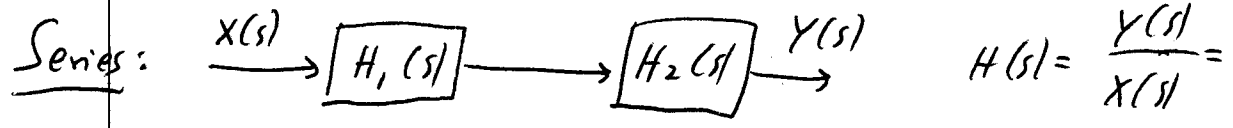Exercise: Plot the poles and zeros in the s-plane for the 5 systems on page 3.

Connecting systems together: (See Section 7.6 in text)



$$H(s) = \frac{Y(s)}{X(s)} = \frac{H_1(s)}{1 + H_1(s) \cdot H_2(s)}$$