


## Frequency Response

The frequency response  $H(\omega)$  of a system is a complex number for each frequency  $\omega$  (rad/sec.).

Polar form  $\Rightarrow H(\omega) = |H(\omega)| \angle H(\omega)$

What does  $H(\omega)$  tell us about a system?

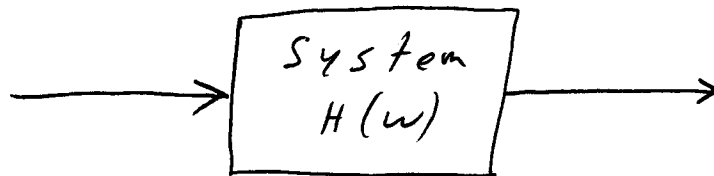Consider applying an input signal to the system that is a cosine with frequency  $\omega_0$ :




Time Signal:  $A \cos[\omega_0 t] \quad \underline{\quad \cos[\omega_0 t + \underline{\quad}] \quad}$

Phasor:  $A \angle 0^\circ$

$\therefore H(\omega)$  describes the "amplitude gain" and the "phase shift" of the system at each frequency  $\omega$ .

(2)

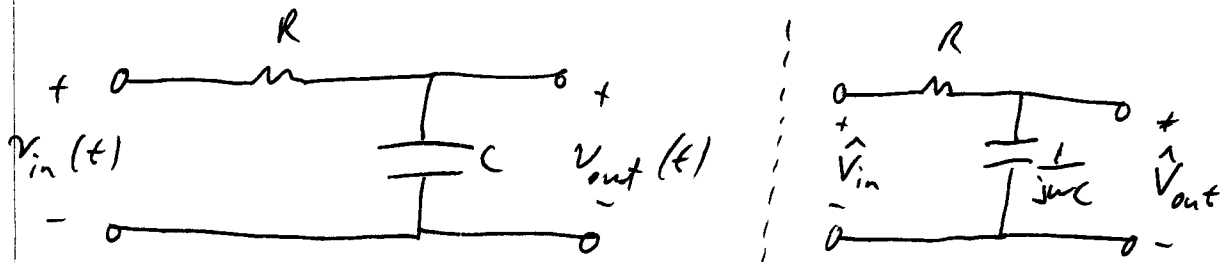Example: Consider the RC circuit that we demonstrated in class.



$$\hat{V}_{out} = \frac{1/j\omega C}{R + \frac{1}{j\omega C}} \hat{V}_{in} = \left( \frac{1}{1 + j\omega RC} \right) \hat{V}_{in}$$

$$H(\omega) = \frac{\hat{V}_{out}}{\hat{V}_{in}} = \frac{1}{1 + j\omega RC}$$

For the values we considered in class:

$$R = 1.1 \text{ k}\Omega$$

$$C = 0.22 \text{ }\mu\text{F}$$

$$\omega = 2\pi \cdot 658 \text{ rad/sec.}$$

$$H(2\pi \cdot 658) = \frac{1}{1 + j1} = \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$= 0.707 \angle -45^\circ$$

$$v_{in}(t) = 0.1 \cos(2\pi \cdot 658t)$$

$$\hat{V}_{in} = 0.1 \angle 0^\circ$$

$$v_{out}(t) = 0.0707 \cos(2\pi \cdot 658t - 45^\circ)$$

$$\hat{V}_{out} = 0.0707 \angle -45^\circ$$