

## Homework Assignment #5 – due via Moodle at 11:59 pm on Monday, Nov. 3, 2025


**Instructions, notes, and hints:**

You may make reasonable assumptions and approximations to compensate for missing information, if any. Provide the details of all solutions, including important intermediate steps. You will not receive credit if you do not show your work.

The first few problems will be graded and the rest will not be graded. Only the graded problems must be submitted by the deadline above. Do not submit the ungraded problems.


**Graded Problems:**

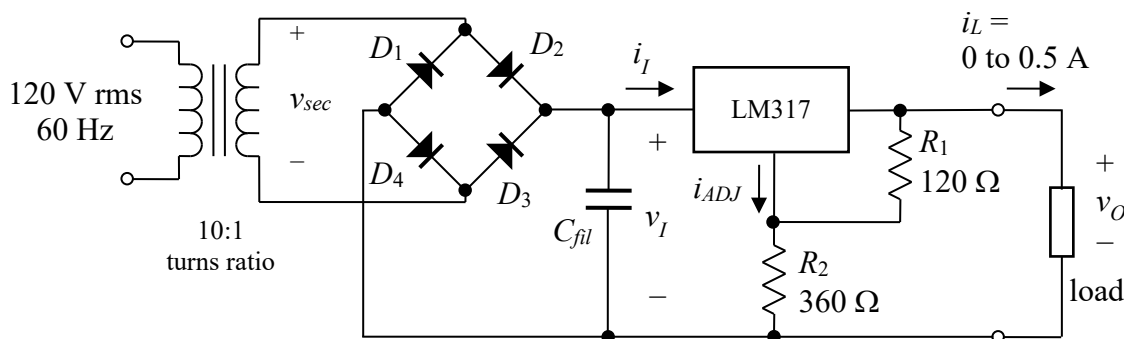1. As shown below, an LM317 voltage regulator is used in a power supply circuit that includes a full-wave bridge rectifier and a filter capacitor  $C_{fil}$ . The rectifier diodes each have a turn-on voltage of  $V_F = 1.0$  V, and the transformer's specified secondary winding voltage is 12 Vrms. The values of resistors  $R_1$  and  $R_2$  have been set to produce a nominal output (load) voltage of  $v_O = 5.0$  V. The largest expected load current is 500 mA. The drop-out voltage  $V_{DO}$  of the regulator is about 2 V. A datasheet for the LM117 and LM317 is available on the Laboratory page at the ECEG 350 course web site.
  - a. By KCL, if the current  $i_{ADJ}$  in the common terminal of the regulator is negligible, then the input current  $i_I$  to the regulator circuit must be approximately the same as the load current  $i_L$  for large values of load current. About 10 mA flows through  $R_1$  and  $R_2$  at all times. Find the required value of capacitor  $C_{fil}$  so that the minimum voltage  $V_{min}$  across the capacitor is roughly 80% greater than  $v_O + V_{DO}$ .
  - b. Find the worst-case ripple on the capacitor voltage for the case when the load draws a DC output current at the maximum value of 0.5 A. Assume that  $C_{fil}$  has the value found in part a.
  - c. Find the approximate time-average power dissipation of the LM317 at full output current ( $i_L = 500$  mA).
  - d. Use the information given in the datasheet to express the load regulation in mV/mA. Assume a typical case at 25 °C for the TO-220 package. Note that the data are given for an output current ranging from 10 mA to  $I_{MAX} = 1.5$  A.




(continued on next page)

 2. In the power supply circuit shown below, a three-terminal regulator provides a nominal voltage of 5 V to an amplifier module. Because of poor design technique, the circuit board trace between the output terminal of the regulator and the positive power supply terminal (the circle near the positive side of  $v_O$ ) is too thin and has an equivalent resistance of  $0.8\ \Omega$ . It is modeled as  $R_t$  in the diagram. The regulator itself has a specified load regulation of  $0.008\ \text{mV/mA}$ . Find the load regulation of the power supply circuit as a whole (i.e., including the effect of  $R_t$ ). The rectifier diodes each have a turn-on voltage of  $1.0\ \text{V}$ , and the power supply is designed to provide up to  $500\ \text{mA}$  of current to the load. The current  $i_{com}$  (like  $i_{ADJ}$  in an adjustable regulator) is negligibly small.



3. For the power supply circuit considered in the previous problem, find:
- the approximate ripple voltage across the filter capacitor  $C_{fil}$  at the maximum load current ( $500\ \text{mA}$ ).
  - the approximate time-average power dissipated by the three-terminal regulator.
  - the line regulation expressed in the  $\%/V$  unit, assuming that measurements reveal an output voltage ripple of  $10\ \text{mV}$  at the maximum load current of  $500\ \text{mA}$ .
4. Convert the line regulation specification  $0.05\%/V$  to the  $\text{mV/V}$  unit for the case when the nominal output voltage of a regulator is  $12\ \text{V}$  and the maximum load current is  $500\ \text{mA}$ .
5. The datasheet for the LM7805 fixed voltage regulator specifies the typical load regulation under the two different conditions listed below. The value given is the change in voltage over the specified change in output current. For each condition, express the load regulation in the  $\text{mV/mA}$  unit. Speculate on why two different results are obtained.
- Load regulation is  $9.0\ \text{mV}$  for output current variation from  $5\ \text{mA}$  to  $1.5\ \text{A}$
  - Load regulation is  $4.0\ \text{mV}$  for output current variation from  $250\ \text{mA}$  to  $750\ \text{mA}$ .
6. The NMOS device in the circuit shown on the next page has the parameter values  $k_n = 1.0\ \text{mA/V}^2$ ,  $V_t = 1.0\ \text{V}$ , and  $\lambda = 0$ . (Parameter  $\lambda$  is related to the channel length modulation effect. If  $\lambda = 0$ , then the drain current is constant in the saturation region for any  $v_{DS}$  value.)
- Determine the region of operation of the MOSFET, and find the values of the drain-to-source voltage  $v_{DS}$  and drain current  $i_D$ . *Hint:* The solution of a quadratic equation might be necessary.
  - Suppose that the drain resistor  $R_D$  is changed to  $500\ \Omega$ . Determine (and confirm) the region of operation, and find the new values of  $i_D$  and  $v_{DS}$ .

(continued on next page)

 


**Circuit diagram for Graded Prob. 6**

### Ungraded Problems:

The following problems will not be graded, but you should attempt to solve them on your own and then check the solutions. Do not give up too quickly if you struggle with one or more of them. Move on to a different problem and then come back to the difficult one after a few hours.

 
1. The power supply circuit shown below is typical of those used to drive high-voltage circuits. Note that it uses a step-up transformer. Also note that the output voltage  $v_O$  is the sum of the two capacitor voltages. The load has a minimum equivalent resistance of  $400\ \Omega$ , but it could be higher. ( $R_{L\min}$  is associated with the maximum possible load current. Smaller load currents correspond to larger equivalent load resistances.) Complete the following analysis steps:
  - a. Find the peak value of the secondary voltage  $v_{sec}$  of the transformer.
  - b. Find the peak voltages across capacitors  $C_1$  and  $C_2$  if  $D_1$  and  $D_2$  are silicon diodes with turn-on voltages that are negligible compared to the secondary voltage.
  - c. Find the approximate nominal output voltage  $v_O$  if the ripple voltage is negligibly small. *Hint:* This circuit called a *voltage doubler*, but you must show/explain why.
  - d. Find the worst-case ripple voltage at the output (across the load  $R_L$ ). The diodes conduct for only a tiny fraction of each period of the secondary voltage.
  - e. Find the peak reverse-bias voltage experienced by each diode, assuming in this case that the voltages across  $C_1$  and  $C_2$  have negligible ripple.




(continued on next page)

2. Show that the expression for  $dv_O/di_L$  for any TEC like the one shown below right is equal to the negative of the Thévenin equivalent resistance; that is, prove the expression shown below left. Note that  $dv_O/di_L$  is equal to the load regulation for a voltage regulator circuit if the minus sign is ignored. Also note that  $dv_O/di_L = \Delta v_O/\Delta i_L$  for the case of a purely resistive (real-valued) load and a purely resistive Thévenin equivalent impedance.

$$\frac{dv_O}{di_L} = -R_{TH}$$

 

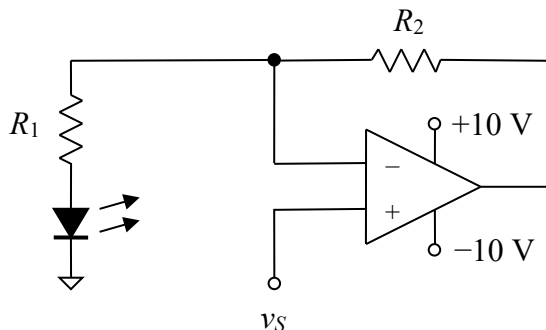3. The circuit shown below is designed to light the LED when voltage  $v_S$  (“S” subscript for “sense”) is above the turn-on voltage of the LED, which is  $V_F = 1.8$  V. The LED shines brighter as  $v_S$  rises. However, above a certain value of  $v_S$  the LED stops increasing in brightness as  $v_S$  continues to rise. Assuming that the constant-voltage model applies for the LED, find the standard 5% values of  $R_1$  and  $R_2$  that would cause the LED to reach its maximum brightness at around  $v_S = 5.0$  V and so that the maximum current through the LED is around 25 mA. The op-amp has the specifications given next to the figure. *Hint:* Aspects of the problem that do not have a significant impact on the determination of the resistor values can be ignored.



Op-Amp:  
 max. input offset voltage magnitude: 8.0 mV  
 max. input bias current: 100 nA  
 typ. open-loop voltage gain:  $1.5 \times 10^5$   
 output voltage limits:  $\pm 9.0$  V  
 output current limit: 35 mA