 



Sequential Logic and Flip-Flops



A clock is (usually) included so outputs are computed at discrete times.


Fig. 12.34 General sequential-logic circuit.

SR Flip-Flop:

 

Present Inputs		Present Output	next output ↓	
$S(t)$	$R(t)$	$Q(t)$	$Q(t+1)$	$\bar{Q}(t+1)$
0	0	0		
0	0	1		
0	1	0		
0	1	1		
1	0	0		
1	0	1		
1	1	0		
1	1	1		

Clocked SR:

 


- Truth table
- How to add asynchronous PRESET and CLEAR ?

Interesting case for clocked SR FF:

$$S=R=1, CLK=1 \Rightarrow Q = \underline{\hspace{1cm}} \quad \bar{Q} = \underline{\hspace{1cm}}$$

What happens when $CLK=0$ with $S=R=1$?

Timing Diagram:

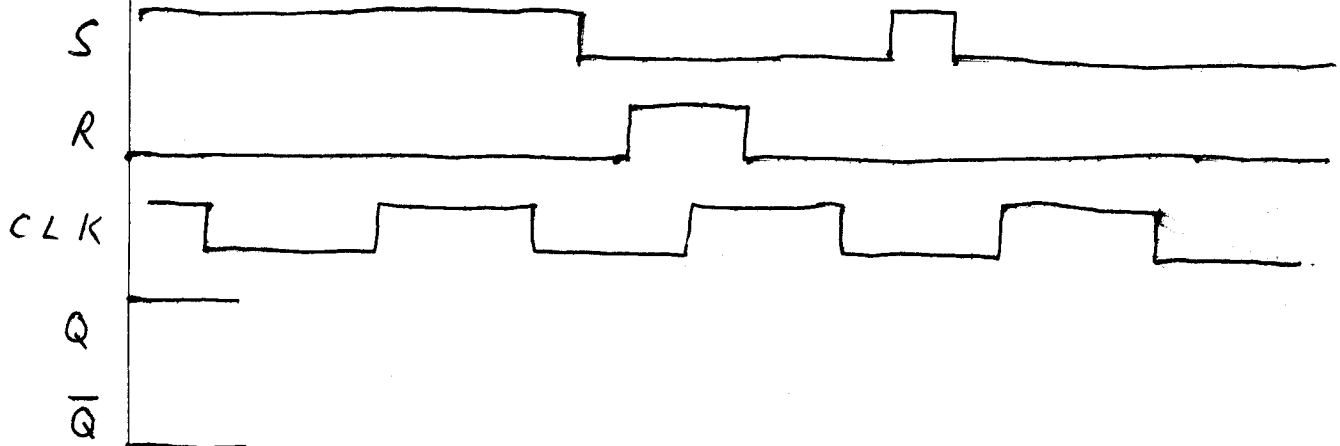

We use clocked SR FF to build other FFs (D, JK)

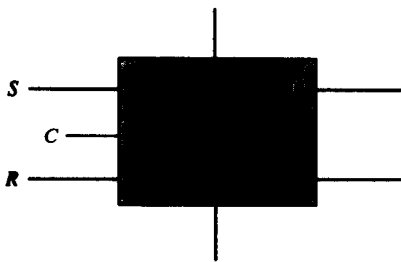


Fig. 12.39 An SR flip-flop with clear and preset inputs.



Fig. 12.40 A D flip-flop.


 


Fig. 12.41 Circuit symbol of a D flip-flop.

Timing for D FF:

 

"Level triggered"
(not "edge triggered")