

Fig. 2.13 Model and circuit symbol of an ideal amplifier having gain A .

Example 2.7

Let us find v_o for the ideal amplifier circuit shown in Fig. 2.14a. The explicit form of this circuit is shown in Fig. 2.14b.

In the circuit given in Fig. 2.14, the noninverting input is at the reference potential, that is, $v_2 = 0$ V. Furthermore, since node v_s and node v_o are constrained by voltage sources (independent and dependent, respectively), in using nodal analysis we sum

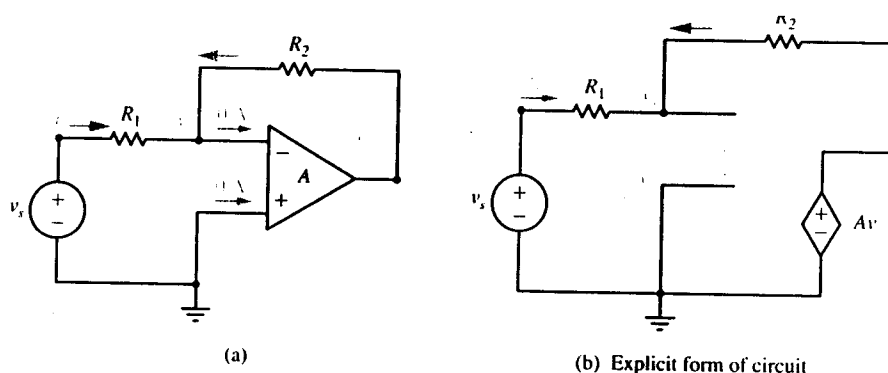


Fig. 2.14 (a) Ideal-amplifier circuit, and (b) explicit form of the circuit.

currents only at node v_1 (the inverting input). Since the amplifier inputs draw no current, by KCL,

$$i_1 + i_2 = 0$$

By Ohm's law

$$\frac{v_s - v_1}{R_1} + \frac{v_o - v_1}{R_2} = 0 \quad \Rightarrow \quad R_2 v_s = (R_1 + R_2)v_1 - R_1 v_o \quad (2.23)$$

But due to the amplifier, $v_o = A(v_2 - v_1) = -Av_1$, so

$$v_1 = \frac{-v_o}{A} \quad (2.24)$$

and substituting this into Eq. 2.23, we get

$$R_2 v_s = (R_1 + R_2) \frac{-v_o}{A} - R_1 v_o = - \left[\frac{1}{A}(R_1 + R_2) + R_1 \right] v_o$$

Thus,

$$v_o = \frac{-R_2 v_s}{R_1 + (1/A)(R_1 + R_2)} \quad (2.25)$$