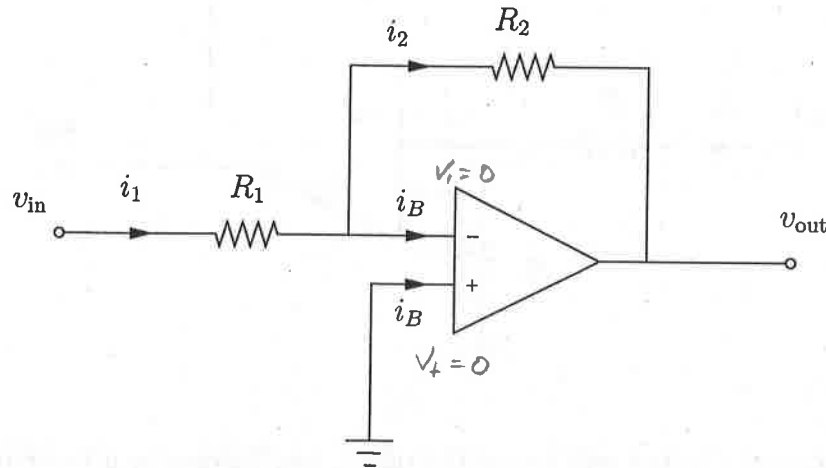


An Example of Non-Ideal Op-Amp Behavior (and a fix)

The inputs to real op-amps do draw some current. Let's consider an op-amp that is ideal in all respects *except* that a constant bias current i_B flows into both the inverting and the non-inverting inputs.



Determine an expression for v_{out} .

Op-amp voltage rule: $V_+ = V_-$

Non-inverting input grounded $\Rightarrow V_+ = V_- = 0$

$$i_1 = \frac{v_{in} - 0}{R_1}$$

Kirchoff Current Law: $i_1 = i_B + i_2 \Rightarrow i_2 = i_1 - i_B$

Ohm's Law: $v_{out} = -i_2 R_2$

$$= -(i_1 - i_B) R_2$$

$$= -\left(\frac{v_{in}}{R_1} - i_B\right) R_2$$

$$= -\frac{R_2}{R_1} v_{in} + i_B R_2$$

↑ Gain of ideal inverting amplifier offset


Consequences:

If $i_B = 100 \text{ nA}$
 $= 0.1 \mu\text{A}$

$R_2 = 100 \text{ k}\Omega$

$i_B R_2 = 10^{-7} \times 10^5$
 $= 0.01 \text{ V}$
 $= 10 \text{ mV}$

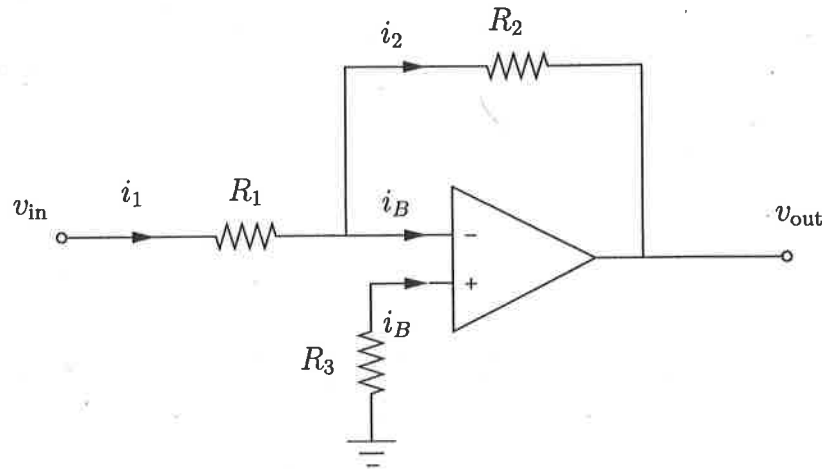Consider the illustrated "fix." The bias current flowing through R_3 will result in a non-zero voltage v_2 at the inverting input. With a proper choice of R_3 we can cancel the offset in the output that results from the non-zero bias current:



Determine the value of R_3 that will cancel the offset, i.e., determine a value of R_3 that will make the output

$$v_{out} = -\frac{R_2}{R_1} v_{in}$$

as it was for an ideal op-amp.

$$V_+ = -i_B R_3$$

$$\Rightarrow V_- = -i_B R_3$$

$$\Rightarrow i_1 = \frac{(V_+ + i_B R_3)}{R_1}$$

$$\text{KCL: } i_2 = i_1 - i_B$$

$$V_{out} = V_- - i_2 R_2$$

$$= -i_B R_3 - (i_1 - i_B) R_2$$

$$= -i_B R_3 - i_1 R_2 + i_B R_2$$

$$= -i_B R_3 - \frac{(V_+ + i_B R_3) R_2}{R_1} + i_B R_2$$

$$= -\frac{R_2}{R_1} V_+ + i_B \left(R_2 - R_3 - \frac{R_3 R_2}{R_1} \right)$$

gain of ideal non-inverting amp

Choose R_3 to make this $\rightarrow 0$.

$$R_2 - R_3 - \frac{R_3 R_2}{R_1} = 0$$

$$R_2 = R_3 \left(1 + \frac{R_2}{R_1} \right)$$

$$R_3 = \frac{R_2}{1 + \frac{R_2}{R_1}}$$

$$= \frac{R_1 R_2}{R_1 + R_2}$$

This is the R_3 of Fig. 10.4 in lab manual.