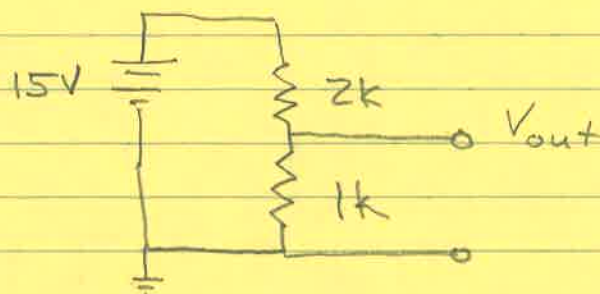


## Finding Thévenin equivalent circuits

### In-class examples 1/24/19

Example 1:

Voltage divider




To find  $V_{th}$  measure the open-circuit voltage across the outputs. In other words, use a good voltmeter (high-resistance - draws no current).

$$V_{o.c.} = V_{th} = \frac{1k}{1k + 2k} V_{in} = 5V$$

Ideal voltage divider result.

Method A for  $R_{th}$ :

Find the short circuit current

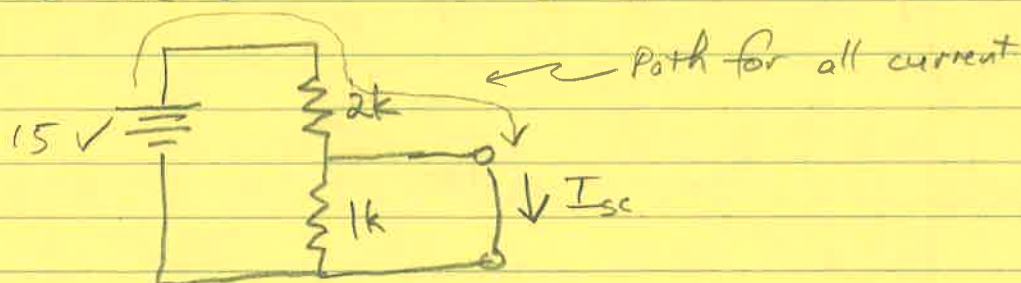

$$I_{sc} = \frac{15V}{2k} = 7.5mA$$

Now use  $R_{th} = \frac{V_{o.c.}}{I_{s.c.}}$

$$\Rightarrow R_{th} = \frac{5}{15/2} = \frac{2}{3} \Omega$$

Method B for  $R_{th}$ :


Replace battery(s) with short-circuit(s) and measure the resistance at the outputs.




⌈ This is actually a parallel combination of the resistors.

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = \frac{1 \times 2}{1 + 2} = \frac{2}{3} \Omega$$

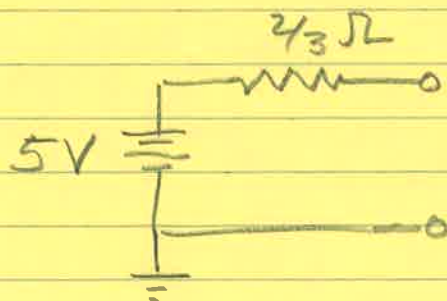Equivalent circuit to our original circuit is



## Example 2

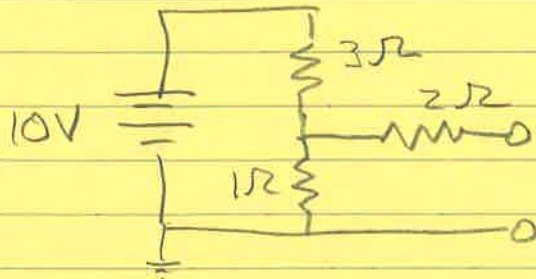


When the outputs are an open circuit no current flows through  $2\Omega$  resistor, so  $\Delta V_{2\Omega} = 0$ , and the measured  $V_{oc}$  is simply the voltage provided by  $3\Omega - 1\Omega$  voltage divider.


$$V_{th} = V_{oc} = 10 \cdot \frac{1}{1+3} = 2.5 \text{ V}$$

## Method A for $R_{th}$ :

If the output is shorted, the circuit is

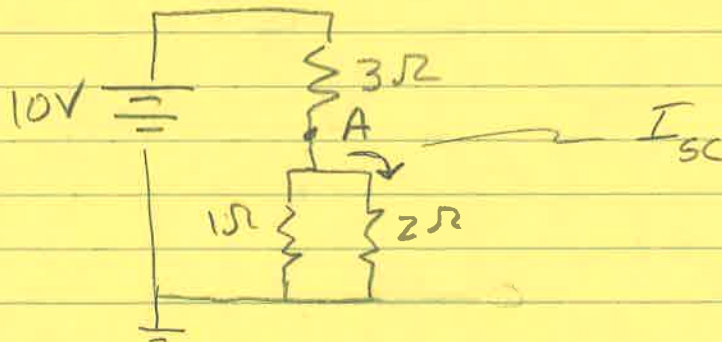

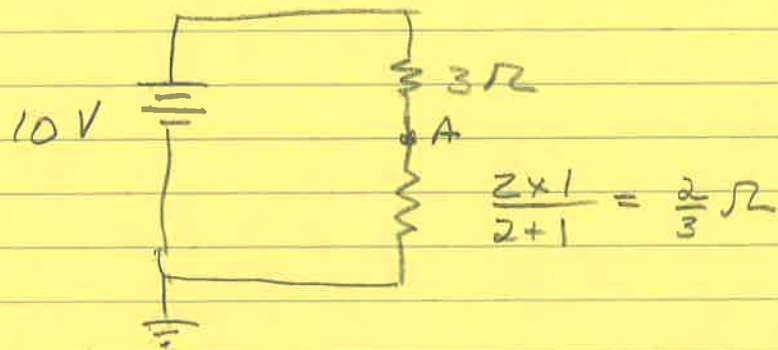To find  $I_{sc}$  we need to know the voltage at A,  $V_A$ . To do this, first find the parallel combination of the  $1\Omega$  &  $2\Omega$  resistors



$$V_A = \frac{\frac{6}{5}}{3 + \frac{6}{5}} \times 10$$

← Voltage divider

$$= \frac{6}{9+2} \times 10$$

$$= \frac{20}{11} V$$

$$I_{sc} = I_{2\Omega} = \frac{V_A}{2} = \frac{10}{11} V$$


$$\Rightarrow R_{Th} = \frac{V_{o.c.}}{I_{s.c.}} = \frac{\frac{5}{2}}{\frac{10}{11}}$$

$$= \frac{11}{4}$$

$$= 2.75 V$$

Method B for  $R_{Th}$ :

Shorting out battery gives

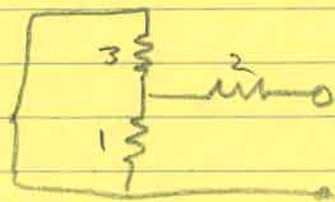

← Parallel combination of 1Ω & 3Ω in series with 2Ω

$$R_{Th} = 2 + \frac{1 \times 3}{1+3} = 2.75 \Omega$$

Thévenin equivalent to our original circuit is

