

Super heterodyne Receiver


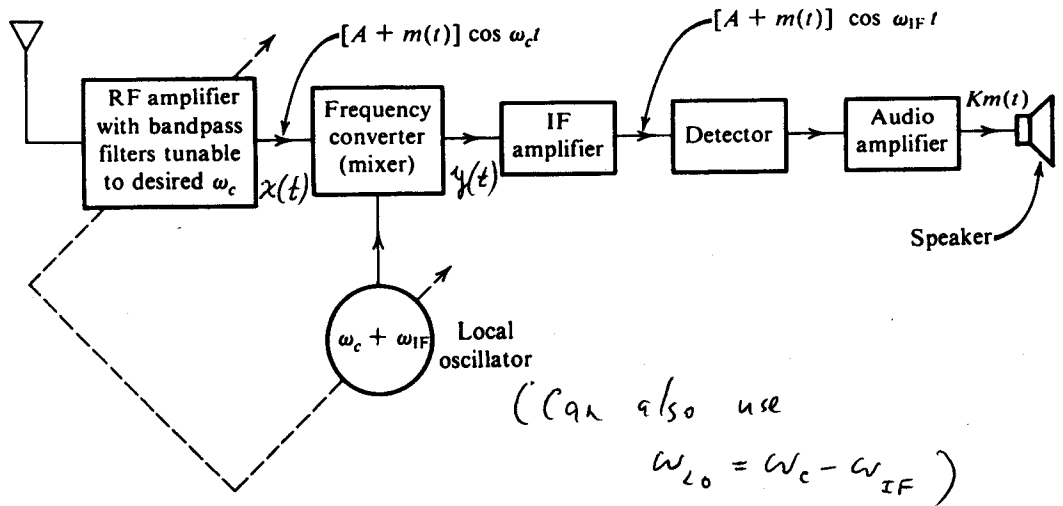


Figure 4.28 Superheterodyne receiver.

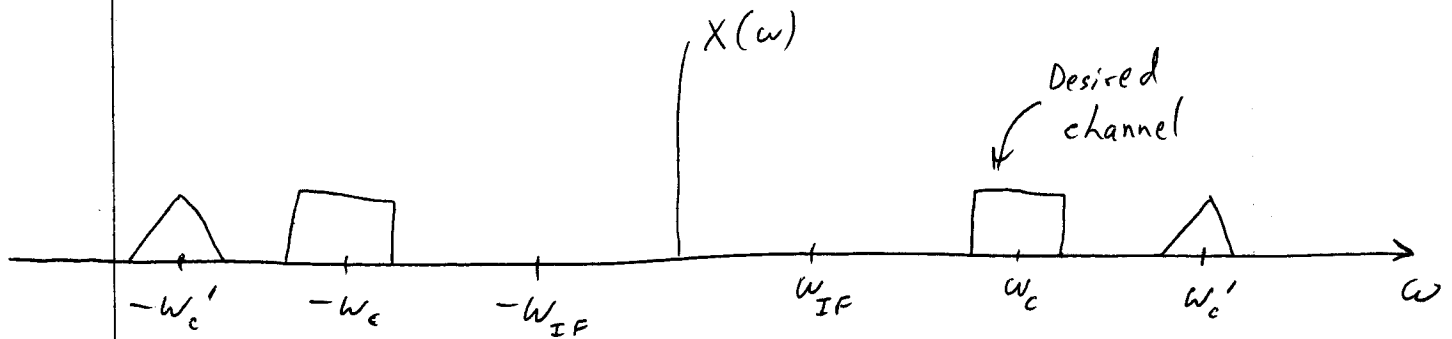

Find $Y(\omega)$ if no RF filter: